### Lab. 02

Logic Design Lab. Spring 2023

Prof. ChangGun Lee

(cglee@snu.ac.kr)

TA. Seonghyeon Park
TA. Jihwan Kim
TA. Hoyong Lee

(rubis.ld.ta@gmail.com)

### **Contents**

- Announcement
- Two-bit comparator
- Xilinx ISE
- Universal Board
- Lab


# Xilinx ISE

## Xilinx ISE Design Suite

- Integrated Synthesis Environment(ISE)
- ISE.


- Release 14.7, 2013
- Features
  - Synthesis(compile) and analysis of HDL<sup>1)</sup> designs.
  - Timing analysis, RTL diagram
  - Xilinx FPGA programmer

## Creating New Project

 


- Select File -> New Project
- Specify Name, Location, Working Directory. Select Top-level source type as Schematic.

## **Project Settings**

 


- Set Project Settings as above
- Click Next → Finish

## **Creating Schematic**

 


- Right-Click anywhere in Hierarchy in Design tab, select New Source.
- New Source Wizard window appears. Select Source Type window, select Schematic and type the File name.
   Ensure Add to project is checked.

# 2-input-AND gate circuit (1)

 


- In Symbols tab, type "and" under Symbol Name Filter.
- Select and2 under Symbols, and place it on board.
- Click I/O Marker button and you can add input/output markers to your circuit.

# 2-input-AND gate circuit (2)

 

- Change the names of input/output symbols.
- Save to apply changes

## Creating Verilog Test Bench

 


- Select New Source by right clicking inside Design tab.
- Select Verilog Test Bench. Type the file name as above.

### Schematic Simulation Code

```
1 // Verilog test fixture created from schematic
     timescale 1ns / 1ps
   module comparator comparator sch tb();
   // Inputs
       reg in1;
9
       reg in2;
10
11 // Output
       wire out1;
13
14 // Bidirs
15
16 // Instantiate the UUT
17
       comparator UUT (
18
          .in1(in1),
19
          .in2(in2),
          .out1(out1)
20
21
   // Initialize Inputs
23
24
       initial begin
          in1 = 0;
25
          in2 = 0;
26
27
         #100;
28
                                                              Wait for 100 ns
          in1 = 0;
29
30
          in2 = 1;
31
          #100;
32
33
          in1 = 1;
          in2 = 0;
34
35
          #100;
36
          in1 = 1;
37
          in2 = 1;
38
39
40 endmodule
41
```


### Simulate Behavioral Model

 

- Save the project
- Ensure that Design tab is selected, View is set to Simulation, and your simulation source code is clicked
- Double click Behavioral Check Syntax for syntax check
- Double click Simulate Behavioral Model

### Simulation Result


🚣 Instan... 🖺 Memory 📔 S 🗤

 


To adjust the view, select View -> Zoom -> To Full View.
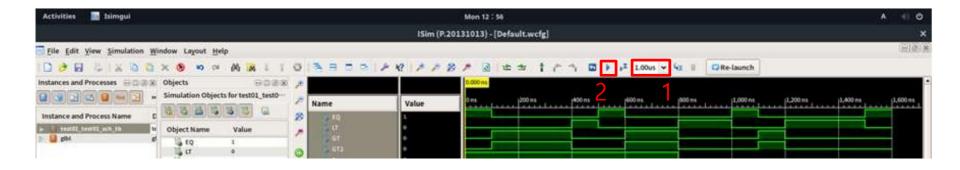
## Tips: Adjust Simulation Time

You can adjust simulation time (default : 1 us)



# Tips: Connecting multiple gates

 

• When connecting multiple gates using 'Add Wire' button, make sure that both two ends don't have I/O markers

## Today's lab

- Implement 2-bit comparator LT, EQ, GT using Xilinx ISE Schematic. Simulate its behavior using Xilinx test bench.
- You may need to adjust simulation time to see every result.
- You should add result in report


## Some problems with Xilinx

- Xilinx ISE program generates log file \*.wdb
  - Sometimes, the file size grows hugely.
  - It makes disk size full, and the disk often fails to boot.
- Don't open multiple simulation windows.
- Before terminating Xilinx ISE program ...
  - Exit your simulation window.
  - Clean up your temp file with Project > Cleanup Project Files

```
ohasno@310-2-26:~/Comparator$ ls -al
total 156
drwxr-xr-x 6 ohasno cseusers 4096 Mar 27 15:43 .
drwx----- 19 ohasno cseusers 125 Mar 27 15:35 ..
-rw-r--r- 1 ohasno cseusers 21792 Mar 27 15:43 comparator_comparator_sch_tb_beh.prj
-rwxr-xr-x 1 ohasno cseusers 21792 Mar 27 15:43 comparator_comparator_sch_tb_isim_beh.exe
-rw-r--r- 1 ohasno cseusers 4709 Mar 27 15:43 comparator_comparator_sch_tb_isim_beh.wdb
-rw-r--r- 1 ohasno cseusers 4359 Mar 27 15:43 Comparator.gise
-rw-r--r- 1 ohasno cseusers 18 Mar 27 15:39 comparator.jhd
-rw-r--r- 1 ohasno cseusers 1908 Mar 27 15:39 comparator.sch
-rw-r--r- 1 ohasno cseusers 0 Mar 27 15:39 comparator.schlog
```


# Universal Board

### Custom-Made Universal Board

 


## Turning it on using power supply


Set voltage to 5V using this button

 
 
## Tips: Look up the datasheet!

- NEVER trust the sorted device boxes... <u>Always check the product</u> <u>name</u> to confirm that you picked the right one.
- Always look up the datasheet online, double check its pin mapping.




 

## Insight

 
#### Xilinx to the rescue!

- Thanks to Xilinx, you don't need to solder or use a breadboard when implementing the circuit.
- In the past, without Xilinx, hardware design was much more challenging than now.



 
#### 1. [TEAM]

Implement 2-bit comparator GT logic on the universal board, using DIP switch and primitive logic gates(INV, AND, OR, XOR, NAND...). Try your best to minimize the number of logic gates/chips used.


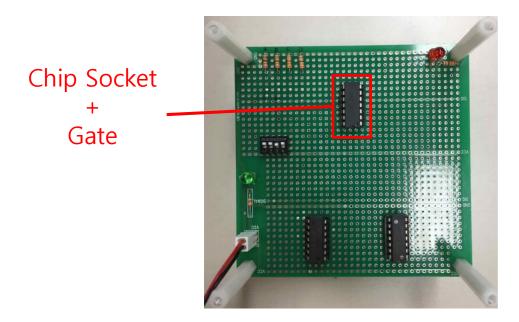
#### Tips

- You should solder chip socket, not on gate directly!
- Remove the sheath from the wire and use it.



#### 2. [Individual]

Draw a circuit diagram for the below formula using ONLY NOR and NOT gates. You can draw it by hand or using any of a computer program.

- 
$$Y = A(B+CD)$$

#### 3. [Individual]

$$Y = AB + ABC + A'B + AB'C$$

- (1) Make a truth table
- (2) Minimize # of operators
- (3) Draw a circuit diagram

- Write a report
  - Either in Korean or in English
  - Your report should include:
    - Lab result (Not only homework)
    - Through discussion
    - Homework (if there is any)
  - # of pages doesn't matter
  - Documents should be submitted as PDF file.
  - Due :

```
Class 001 – April, 17<sup>th</sup> (Before class begin at 7:00pm)
Class 002 – April, 18<sup>th</sup> (Before class begin at 7:00pm)
Class 003 – April, 20<sup>th</sup> (Before class begin at 7:00pm)
```