
 


## 1. Counter module


Simulation result:

 

Here, we check that bcd\_one is incremented by 1 at every positive edge of the clock. And when bcd\_one is 1001 and another positive edge of the clock comes, bcd\_one becomes 0000 and bcd\_ten is incremented by 1.



 When reset=1, both bcd\_ten and bcd\_one are set to 0000.



When bcd\_ten=1001 and bcd\_one=1001, meaning the counter has counted to 99, and another positive edge of the clock comes, both bcd\_ten and bcd\_one are set to 0000.

## 2. Two digit counter

(1) Verilog source code

(i) TDC main:

```

module TDC(
    input clk,
    input reset,
    output [6:0] bcd7_ten,
    output [6:0] bcd7_one
);

    wire new_clk;
    wire [3:0] bcd_ten;
    wire [3:0] bcd_one;

    freq_divider T1(.clr(reset), .clk(clk), .clkout(new_clk));
    counter T2(.clk(new_clk), .reset(reset), .bcd_ten(bcd_ten), .bcd_one(bcd_one));
    bcd_to_7 T3(.bcd(bcd_ten), .seg(bcd7_ten));
    bcd_to_7 T4(.bcd(bcd_one), .seg(bcd7_one));

endmodule

```

It receives clk and reset as input, and gives output for 7-segment display of the ten's digit and one's digit of the counter. It makes an instance of frequency divider to obtain a new clock whose frequency is 1Hz, and gives the new clock as the clock for the counter and the two bcd-to-7-segment decoders. The outputs bcd\_ten and bcd\_one of the counter is given to the decoders as inputs so the BCD value can be converted to 7-segment.

(ii) counter:

```

module counter(

```

```

input clk,
input reset,
output reg [3:0] bcd_ten,
output reg [3:0] bcd_one
);

always@ (posedge clk or posedge reset) begin
    if(reset) begin
        bcd_ten = 0;
        bcd_one = 0;
    end
    else if(bcd_one == 4'b1001) begin
        if(bcd_ten == 4'b1001) begin
            bcd_ten = 4'b0000;
            bcd_one = 4'b0000;
        end
        else begin
            bcd_ten = bcd_ten + 1;
            bcd_one = 4'b0000;
        end
    end
    else begin
        bcd_one = bcd_one + 1;
    end
end

endmodule

```

---

The always statement is triggered at the positive edge of the clock or reset. If reset=1, both outputs are set to 0. If both bcd\_one and bcd\_ten are 9, then both are set to 0. If bcd\_one is 9 and bcd\_ten is not 9, bcd\_one is set to 0 and bcd\_ten is incremented by 1. Otherwise, only bcd\_one is incremented by 1.

(iii) frequency divider:

---

```

module freq_divider(
    input clk,
    input clr,
    output reg clkout
);

    reg[31:0] cnt;

    always@ (posedge clk) begin
        if(clr) begin
            cnt <= 32'd0;
            clkout <= 1'b0;
        end
        else if (cnt == 32'd25000000) begin
            cnt <= 32'd0;
            clkout <= ~clkout;
        end
        else begin
            cnt <= cnt + 1;
        end
    end
end

endmodule

```

---

The frequency divider receives clock and clear as input, and gives another clock as output. It has an internal variable count. The count and the output clock is set to 0 when clear is 1. Then count is incremented by 1 at every positive edge of the input clock. When count reaches 25000000(=25M), the output clock is toggled. So if 50MHz clock is given as input, the output clock is flipped every 0.5s, meaning the period is 1s, meaning the frequency is 1Hz.

(iv) BCD to 7-segment decoder:

---



```
module bcd_to_7(  
    input [3:0] bcd,  
    output reg [6:0] seg  
);  
  
    always@(bcd) begin  
        case(bcd)  
            4'd0: seg <= 7'b0111111;  
            4'd1: seg <= 7'b0000110;  
            4'd2: seg <= 7'b1011011;  
            4'd3: seg <= 7'b1001111;  
            4'd4: seg <= 7'b1100110;  
            4'd5: seg <= 7'b1101101;  
            4'd6: seg <= 7'b1111101;  
            4'd7: seg <= 7'b0000111;  
            4'd8: seg <= 7'b1111111;  
            4'd9: seg <= 7'b1101111;  
        endcase  
    end  
endmodule
```



---

When the input bcd is changed the always statement is triggered, where the output seg is given the 7-segment values of the corresponding BCD value.

(2) Result of implementation



(i) Increasing 1 in normal case

  

  




When the counter is not 99 and reset button is not pressed ( $\text{reset} = 0$ ) it increases by 1 every second. We also check when  $\text{bcd\_one}$  is 9 and 1 second passes,  $\text{bcd\_one}$  becomes 0 and  $\text{bcd\_ten}$  is incremented by 1.

(ii)  $t=100\text{s}$

  

When the counter is 99 and 1 second passes, both  $\text{bcd\_ten}$  and  $\text{bcd\_one}$  are set to 0.

(iii) when  $\text{reset}=1$

   

When the counter is counting, and the reset button is pressed to make  $\text{reset}=1$ , both outputs are immediately set to 1.

#### Discussion

During the Verilog implementation, there was a problem where the clock was oscillating as intended but the counter remained undefined. We found that the problem was because the the always statem

ent in the counter module did not have the positive edge of the reset in its sensitivity list. Adding that to the sensitivity list, we were able to solve the problem. Using `always@ (posedge clk or posedge reset)` we were able to make a counter that is incremented at every positive edge of the clock and is reset when reset becomes 1, independent of the clock timing.